

2 Mode

- ① Minimum mode
- ② Maximum mode


Active High

- $y = 1 \rightarrow ON$
- $y = 0 \rightarrow OFF$

Active Low

- $\bar{y} = 0 \rightarrow ON$
- $\bar{y} = 1 \rightarrow OFF$

Min mode \rightarrow Pin 33 $\rightarrow 1$


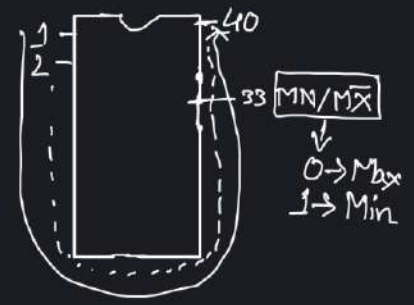


AD0-ADS & /

Multiplexed



Read data:

Step 1: CLK generator

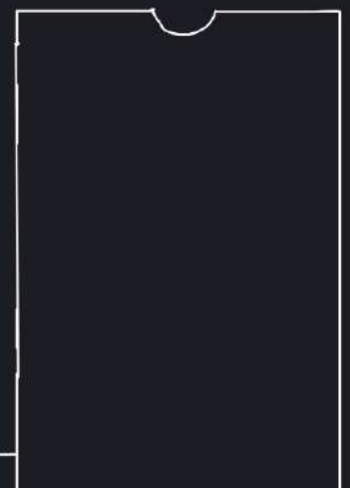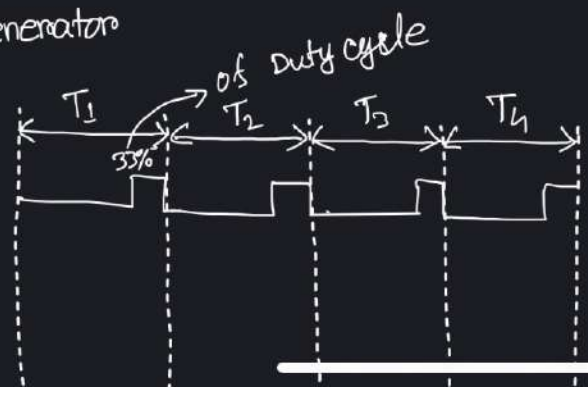

Read data:

Step 1: CLK generator

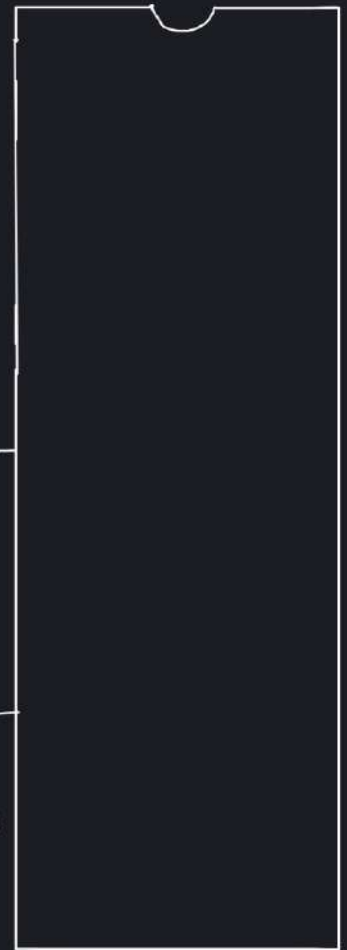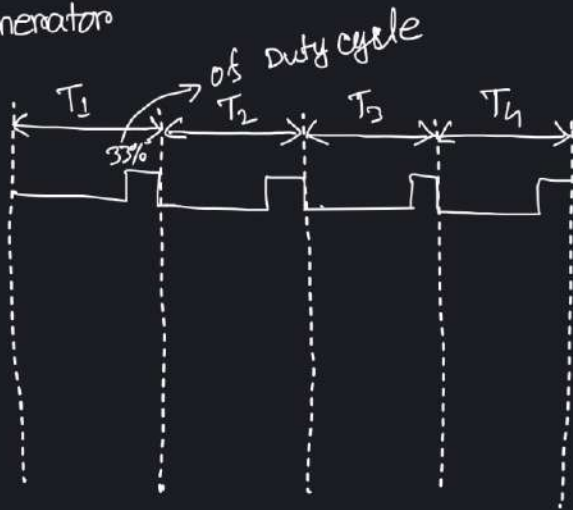

T₁:

① MP 20 bits address generate $\overline{A19}$

② $ALE=1$
($A0-A19$)

T₂:

Prepares all the control signals
 $\overline{MEM}/\overline{IO}$
 \overline{DEN} , \overline{RD}
 \overline{WR} , Ready
 DT/\overline{R}

T₃:

Actually reads or writes the data to MEM or I/O
($D0-D15$)

T₄:

All signals go back to default state

Step 2: Generate 20 bits address from segment offset.
($S4, S3 \rightarrow$ segment Identification)

Segment Identification

MSB	LSB	↓
S4	S3	Segment
0	0	ES
0	1	SS
1	0	CS
1	1	DS

Step 3: Now, the address will be placed on the address line ($A0-A19$) (20 bits)

Step 4: $ALE=1$; activates the latch & stores the 20 bit Address

Step 5: The address/Location will be triggered & data communication process will start


Step 6: $\overline{DEN}=0$; This will activate the Transceiver & activate the data lines ($D0-D15$)



① ALE = 1
(AD-A15)

DEN, RD
WR, Ready
DT/R

470
(D0-D15)

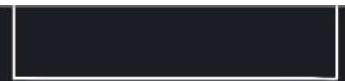

Step 2: Generate 20 bits address from segment offset:
(S4, S3 → segment Identification)


Segment Identification		
MSB	LSB	
S4	S3	Segment
0	0	ES
0	1	SS
1	0	CS
1	1	DS

Step 3: Now, the address will be placed on the address line (AD0-AD19) (20 bits)

Step 4: ALE=1; activates the latch & stores the 20 bit Address

Step 5: The address/Location will be triggered & data communication process will start

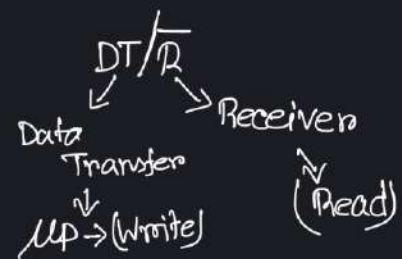Step 6: $\overline{DEN}=0$; This will activate the Transceiver & activate the data lines (D0-D15)



10

Step 7: All the control signals will be prepared for reading from memory

$\overline{DEN}=0$

$\overline{RD}=0$

$\overline{MEM}/\overline{IO}=1$

$\overline{WR}=1$

$\overline{DT}/\overline{R}=0$

Ready=0 (for slow I/O on memory, the value will be 1)

Step 8: Now the actual data (62h) will be read by the μp through (D0-D15)